



Processor Design

–

Arithmetics and Datapath Design

Professor Jari Nurmi
Institute of Digital and Computer Systems
Tampere University of Technology, Finland
email jari.nurmi@tut.fi



Refinement of HW Design Process

- Processor design can start with a very informal description
 - It is useful to describe the functionality of the processor instructions formally on high level using e.g.
 - VHDL
 - SystemC
 - Some register transfer notation (like RTN in Heuring – Jordan)
 - When proceeding in the design process, more details can be added to refine the description
 - We proceed to design the datapath and identify needed control signals
 - Pipelining further refines the processor operation
 - Control part is implemented to generate the ctrl signals
-



Arithmetics Revisited

- Digital number systems
 - Fixed-point arithmetics
-



Digital Number Systems

- Digital number systems have a base or radix b
- Using positional notation, an m -digit base b number is written

$$x = x_{m-1} x_{m-2} \dots x_1 x_0$$
$$0 \leq x_i \leq b-1, 0 \leq i < m$$

- The value of this unsigned integer is

$$\text{value}(x) = \sum_{i=0}^{m-1} x_i \cdot b^i$$



Fractions and Fixed-Point Numbers

- The value of the base b fraction $.f_{-1}f_{-2}\dots f_{-m}$ is the value of the integer $f_{-1}f_{-2}\dots f_{-m}$ divided by b^m
 - The value of a mixed fixed point number
$$X_{n-1}X_{n-2}\dots X_1X_0.X_{-1}X_{-2}\dots X_{-m}$$
is the value of the $n+m$ digit integer
$$X_{n-1}X_{n-2}\dots X_1X_0X_{-1}X_{-2}\dots X_{-m}$$
divided by b^m
 - Moving radix point one place left divides by b
 - For fixed radix point position in word, this is a right shift of word
 - Moving radix point one place right multiplies by b
 - For fixed radix point position in word, this is a left shift of word
-



Negative Numbers, Complements, and Complement Representations

- Complement number systems
 - Represent both positive and negative numbers
 - One's complement
 - Two's complement
 -
 - How to compute the complements
 - Use of complement number systems in signed addition hardware
-



Complement Number Systems

- Complement number systems use unsigned numbers to represent both positive and negative numbers
 - Recall that the range of an m digit base b unsigned number is $0 \leq x \leq b^m - 1$
 - The first half of the range is used for positive, and the second half for negative, numbers
 - Positive numbers are simply represented by the unsigned number corresponding to their absolute value
-



Use of Complements to Represent Negative Numbers

- The complement of a number in the range from 0 to $b^m/2$ is in the range from $b^m/2$ to $b^m - 1$
 - A negative number is represented by the complement of its absolute value
 - There are an equal number (± 1) of positive and negative number representations
 - The ± 1 depends on whether b is odd or even and whether radix complement or diminished radix complement is used
 - We will assume the most useful case of $b = 2$
 - Then radix (2's) complement system has one more negative representation
 - Diminished radix (1's) complement system has equal numbers of positive and negative representations
-



Reasons to Use Complement Systems for Negative Numbers

- The usual sign-magnitude system introduces extra symbols + and - in addition to the digits
 - In binary, it is easy to map 0 \rightarrow + and 1 \rightarrow -
 - In base $b > 2$, using a whole digit for the two values, + and - , is wasteful
 - Most important, however, it is easy to do signed addition and subtraction in complement number systems
-



Negation in Complement Number Systems

- Except for $-b^m/2$ in the 2's complement system, the negative of any m-bit value is also m bits
 - The negative of any number x, positive or negative, in the 2's or 1's complement system is obtained by applying the complement operation to x, respectively
 - 1's complement is taken by simply inverting each bit
 - In 2's complement we need to add 1 to the 1's complement
-



Complement Fractions

- ❑ Since m digit fraction is same as m digit integer divided by b^m , the b^m in complement definitions corresponds to 1 for fractions
 - ❑ Thus 2's complement of $x = .x_{-1}x_{-2}\dots x_{-m}$ is $(1-x) \bmod 1$, where mod 1 means discard integer
 - ❑ The range of fractions is roughly -1 to +1
-



Scaling Complement Numbers by Powers of the Base

- ❑ Roughly, multiplying by b corresponds to moving radix point one place right or shifting number one place left
 - ❑ Dividing by b roughly corresponds to a right shift of the number or a radix point move to the left one place
 - ❑ There are 2 new issues for complement numbers:
 - 1) What is new left digit on right shift?
 - 2) When does a left shift overflow?
-



Right Shifting a Complement Number to Divide by 2

- For positive $x_{m-1}x_{m-2}\dots x_1x_0$, dividing by 2 corresponds to right shift with zero fill

$$0x_{m-1}x_{m-2}\dots x_1$$

- For negative $x_{m-1}x_{m-2}\dots x_1x_0$, dividing by 2 corresponds to right shift with 1-fill

$$(1)x_{m-1}x_{m-2}\dots x_1$$

- So, we feed in the sign bit!
 - This holds for both 2's and 1's complement systems
-



Complement Number Overflow on Left Shift to Multiply by 2

- For positive numbers, overflow occurs if any bit 1 shifts off left end
 - Positive numbers also overflow if the digit shifted into left position makes number look negative
 - For negative numbers, overflow occurs if bit 0 shifts off left end
 - Negative numbers also overflow if new left digit makes number look positive
-




Fixed-Point Addition and Subtraction

- ❑ If the radix point is in the same position in both operands, addition or subtraction act as if the numbers were integers
 - ❑ Addition of signed numbers in radix complement system needs only an unsigned adder
 - ❑ So we only need to concentrate on the structure of an m-bit binary unsigned adder
 - ❑ To see this let x be a signed integer and $\text{rep}(x)$ be its 2's complement representation
 - ❑ The following theorem summarizes the result
Operands are $\text{rep}(x)$ & $\text{rep}(y)$. Then $s = \text{rep}(x+y)$, except for overflow
 - ❑ So, all we need is a binary m-bit adder
-



Base b Radix Complement Subtractor

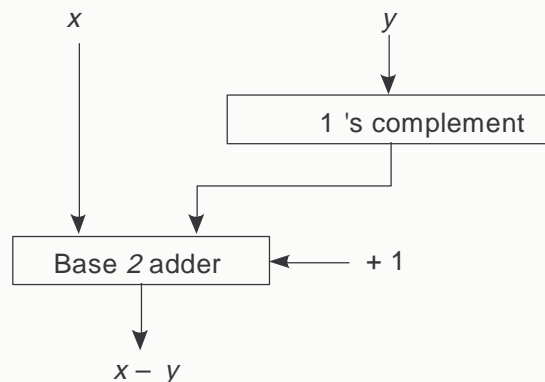- ❑ To do subtraction in the radix complement system, it is only necessary to negate (radix complement) the 2nd operand
- ❑ It is easy to take the diminished radix complement, and the adder has a carry-in for the +1






Overflow Detection in Complement Add and Subtract

- ❑ We saw that all cases of overflow in complement addition came when adding numbers of like signs, and the result seemed to have the opposite sign
- ❑ For even $b=2$, the sign can be determined from the left digit of the representation
- ❑ Thus an overflow detector only needs x_{m-1} , y_{m-1} , s_{m-1} , and an add/subtract control



2's Complement Adder/Subtracter

 - ❑ A multiplexer to select y or its complement becomes an exclusive OR gate





Speeding up Addition

- One way or another speed up the carry chain

 - Carry look-ahead
 - calculate the propagate/generate information
 - decision of the carry-out from each bit can be then done locally
 - Carry-skip
 - calculate the propagate/generate information
 - use it to effectively cut the carry chain by skipping sections
 - Carry-select
 - pre-calculate both with carry-in = 0 and =1
 - choose the right when carry known (block-wise)
-




Binary Propagate and Generate Signals


- In binary, the generate for digit j is $G_j = x_j \cdot y_j$
 - Propagate for digit j is $P_j = x_j + y_j$
 - Of course $x_j + y_j$ covers $x_j \cdot y_j$ but it still corresponds to a carry out for a carry in
 - Carries can then be written: $c_1 = G_0 + P_0 \cdot c_0$
 - $c_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot c_0$
 - $c_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot c_0$
 - $c_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0$
 - In words, the c_2 logic is: c_2 is one if digit 1 generates a carry, or if digit 0 generates one and digit 1 propagates it, or if digits 0 and 1 both propagate a carry-in
-



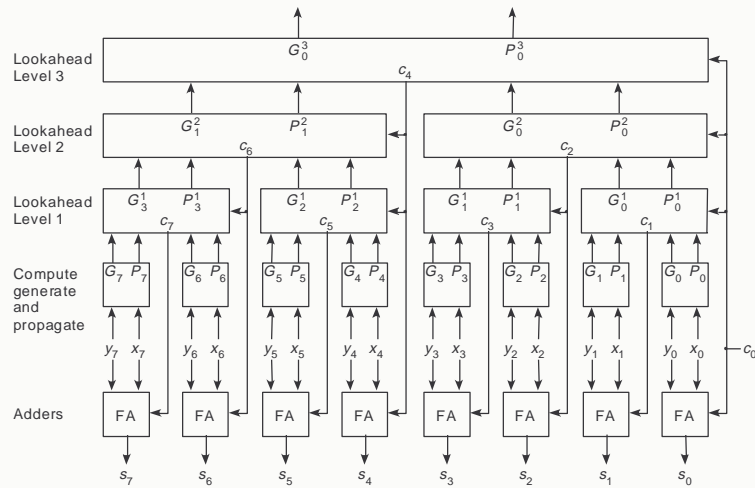Carry Lookahead Adder for Group Size $k = 2$



Digital Multiplication Schema

 


p: product

pp: partial product



 Parallel Array Multiplier for Unsigned Numbers




Signed Multiplication

- The sign of the product can be computed immediately from the signs of the operands
- For complement numbers, negative operands can be complemented, their magnitudes multiplied, and the product recomplemented if necessary
- A complement representation multiplicand can be handled by a 2's complement adder for partial products and sign extension for the shifts



2's Complement Multiplier Hardware

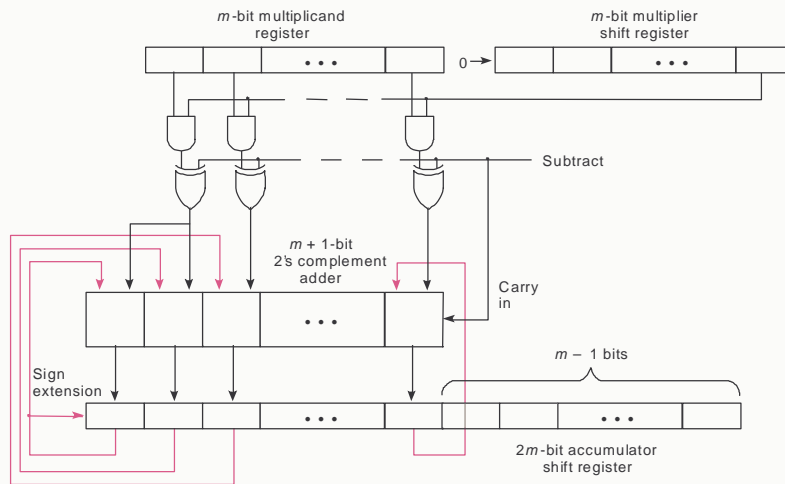

A 2's Complement Integer's Value Can Be Represented as:

$$\text{value}(y) = -y_{m-1} 2^{m-1} + \sum_{i=0}^{m-2} Y_i 2^i$$


This means that the value can be computed by **adding** the weighted values of all the digits except the most significant, and **subtracting** that digit.



Exploration of Architecture Alternatives




1-bus SRC (Simple RISC)

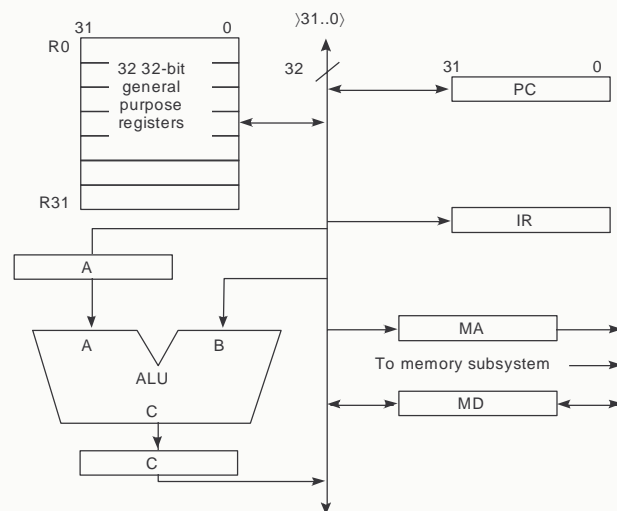

Source: Heuring – Jordan: Computer Systems Architecture and Design




2-bus SRC (Simple RISC)

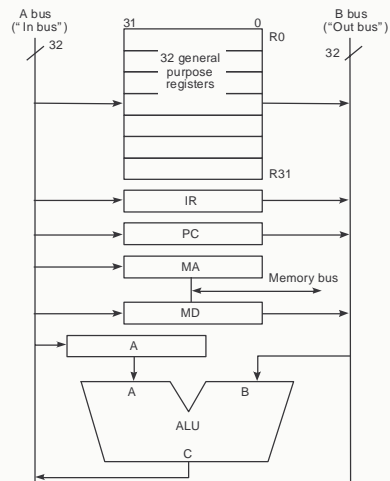

Source: Heuring – Jordan: Computer Systems Architecture and Design



3-bus SRC (Simple RISC)

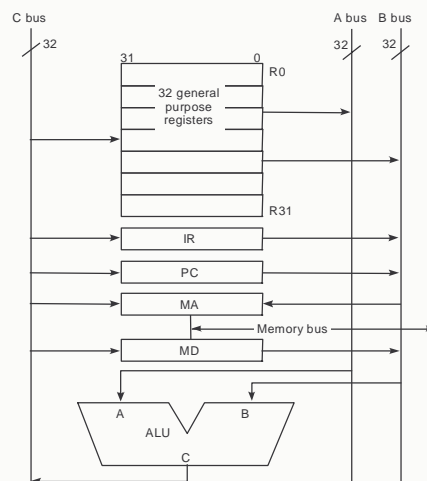


Source: Heuring – Jordan: Computer Systems Architecture and Design




The CPU–Memory Interface: Memory Address and Memory Data Registers, MA<31...0> and MD<31...0>

 
- MD is loaded from memory or from CPU bus



- MD can drive CPU bus or memory bus

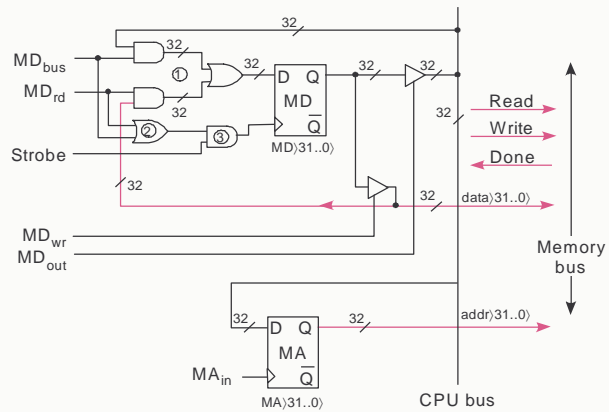


Construction of Datapath

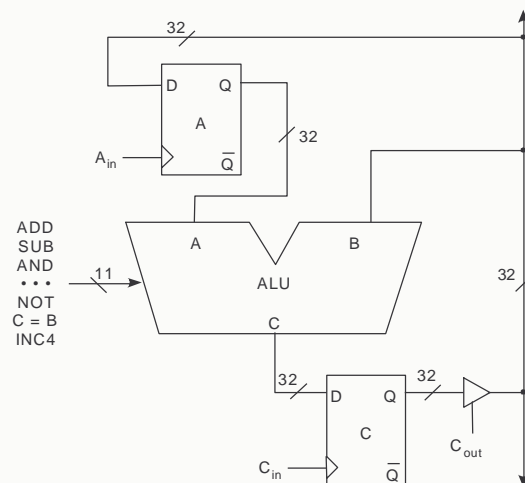



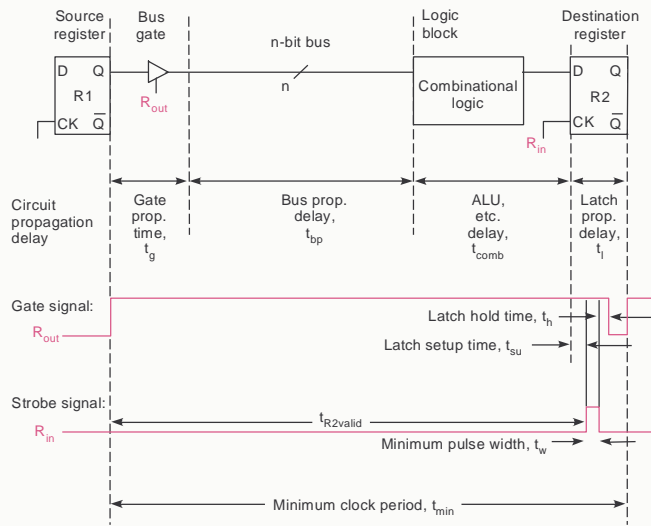Clocking the Data Path: Register Transfer Timing



□ $t_{R2valid}$ is the period from begin of gate signal till inputs to R2 are valid

□ t_{comb} is delay through combinational logic, such as ALU or cond logic



Effect of Signal Timing on Minimum Clock Cycle

□ A total latch propagation delay is the sum

$$T_l = t_{su} + t_w + t_h$$

- All above times are specified for latch
- t_h may be very small or zero

□ The minimum clock period is determined by finding longest path from ff output to ff input

- This is usually a path through the ALU
- Conditional signals add a little gate delay

□ Using this path, the minimum clock period is

$$t_{min} = t_g + t_{bp} + t_{comb} + t_l$$



Implementation Issues 1

□ Registers vs. Latches

- Latch is only about $\frac{1}{2}$ of the FF complexity
- Transparency may cause malfunctions in the presence of feedback
- Testability or technology selections may restrict latch usage

- However, master-slave FF can be made up from two latches
- Requires two-phase **non-overlapping** clocking
- Useful in retiming critical paths (separation of M and S latches!)

- Other clocking schemes may be used with edge-triggered FFs
- D-type of FF is most useful from complexity point of view
- SR, JK, T flip-flops can be easily constructed from DFF if needed



Implementation Issues 2


□ Tri-states vs. multiplexers

E	A	F
0	0	Z
0	1	Z
1	0	0
1	1	1



Tri-state buffer


S	A	B	F
0	0	x	0
0	1	x	1
1	x	0	0
1	x	1	1

 

2-input multiplexer



□ Bus implementation

 

Implementation Issues 3

□ Target technology impacts

- FPGA restrictions
 - Tri-states may not be available
 - Latches should be avoided
 - Asynchronous operation may fail because of routing delays
- CMOS ASIC technologies
 - Tri-state is the default for electrical bus interface
 - Latches may be allowed
 - Input latching for low power
 - Division of MS-flip-flops to two latch distributed stages
 - "Latch-file"
 - Testability issues may still restrict the use of latches
 - Asynchronous operation better under control
 - Proportion of routing delays vs. gate delays a function of line width
 - Floorplan, routing plan, layer allocation well under designer control



Implementation Issues 4

Bus signalling

- Conventional voltage-level based bus
 - Current-mode bus
 - DS-CDMA bus
-



End of Datapath Design

next we will look at pipelining
and other forms of parallelism
